

# Remote power supply for MiniTiouners

## Why this additional board?

For the users of the F1CHF MiniTiouner V1, and the F5XG batch, as well as the BATC version V2, it was not possible to control the LNB's remote power supply via Jean-Pierre F6DZP's Minitioune V0.8s software.

## Description hardware

I developed an additional card (32 \* 41mm) using as in the MiniTiounerPro the chip [RT5047](#) from [RICHTEK](#), a highly integrated voltage regulator and interface IC. It fit on top of the existing Minitiouner board designed by [F1CHF](#) thanks to the fixing holes having the same spacing.



Figure 1 3D picture top

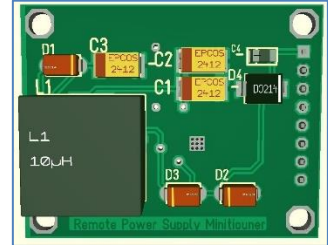


Figure 2 3D picture bottom

The schematic is simply what is described in the datasheet.

Nothing special, except that it is necessary to use Schottky diodes, this is mandatory for D1 in particular.

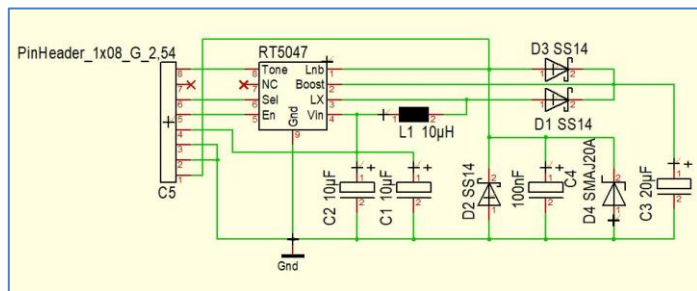


Figure 3 The schematic

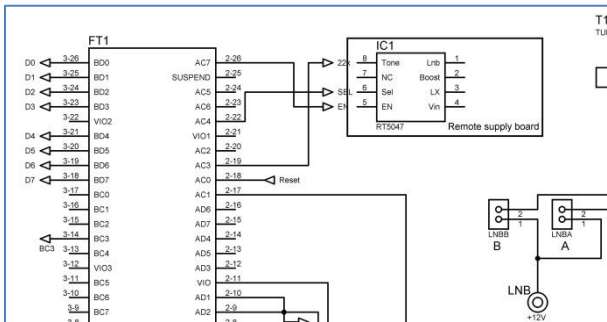


Figure 4 How to connect

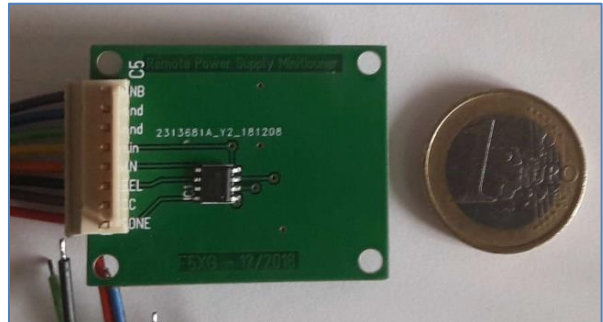


Figure 5 RT5047 Board

## Software

I asked Jean-Pierre F6DZP for the upgrade possibility like with MiniTiounerPro, in the Expert mode to drive per software LNB voltages, 22kHz & (why not?) Fplug while having on hand a MiniTiouner. (See Figure 6 Screenshot options of LNB, Fplug & 22kHz)

He answered: "Yes I can do it ....but, In one future software development via the mintioune.ini file, I will add the choice of external module RT5047 in order to drive these options."

And he did it! Thank you Jean-Pierre.

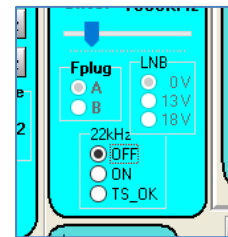


Figure 6 Screenshot options of LNB, Fplug & 22kHz

# Remote power supply for MiniTioners

UPDATE June 2019

Jean-Pierre F6DZP has put online the software version MinitiouneV09beta8\_9 package.

The BATC MiniTioner V2 is recognized by this new software, BUT not the F1CHF / F5XG MiniTioner card.

The FUTURE online software now will correct this problem also for MiniTioner version V1 (NB I tested it).

WARNING .... The 22kHz signal is to be recovered on the pin:

- 12 of the NIM for the F1CHF MiniTioner V1 card, and of the same batch F5XG
- 40 of the NIM for BATC MiniTioner V2 Card

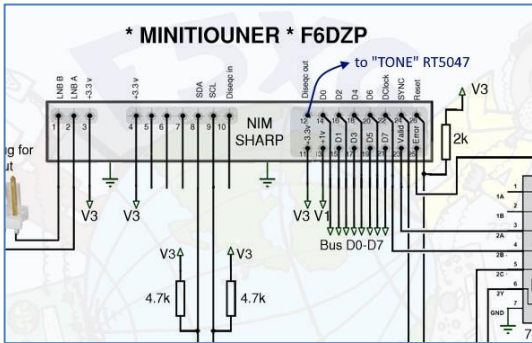


Figure 7 Extract diagram NIM SHARP V1

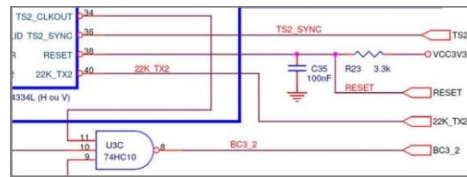


Figure 8 Extract diagram NIM V2 BATC

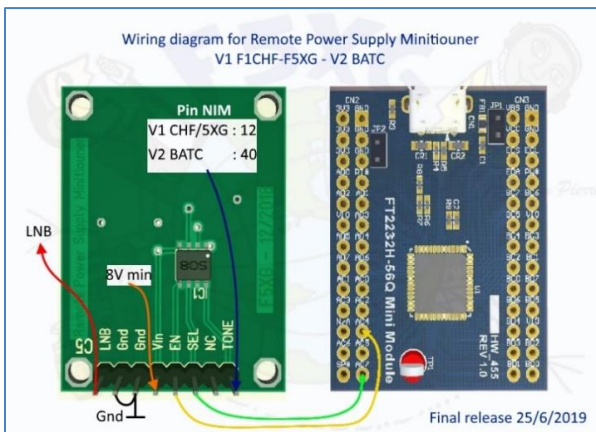


Figure 9 Card Connections V1 et V2

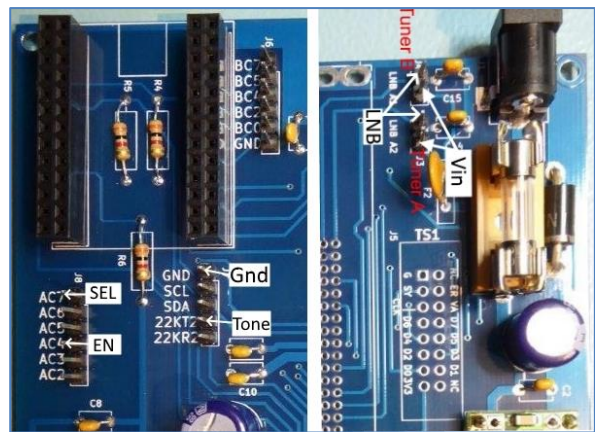


Figure 10 Card Connections V2 BATC

## Remote power supply for MiniTioners

### Card wiring V1

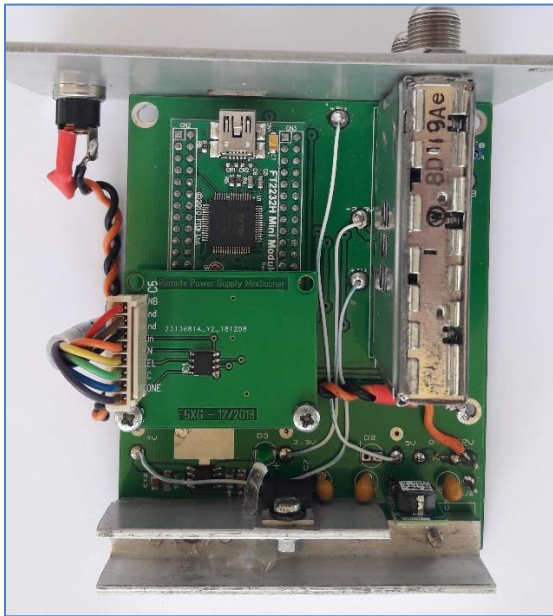


Figure 11 the board in place

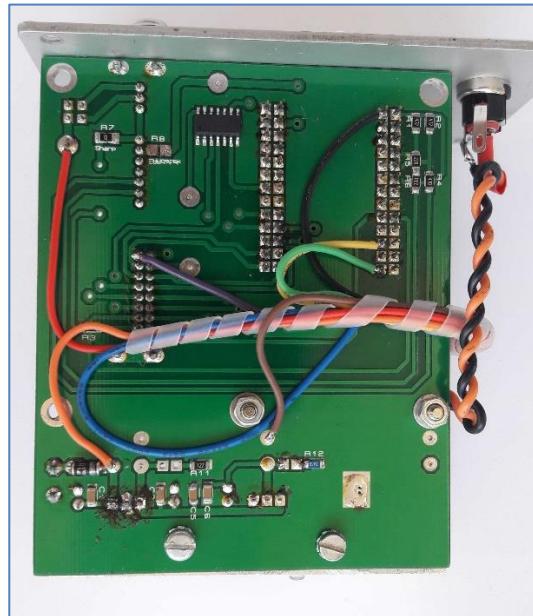


Figure 12 wiring

### Card wiring V2

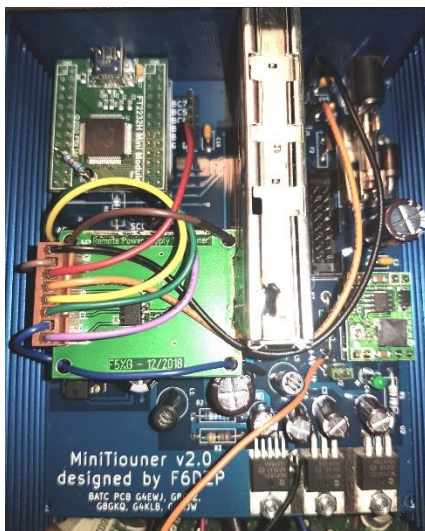


Figure 13 implementation ON8GE Pierre



Figure 14 implementation 2WØDS Dale

### Conclusion

Everything is working properly on V1 and V2 cards. (Watch [video](#) from Dale 2WØDS)

The RT5047 receives the 22kHz signal driven by the NIM commands, and generated in the latter: 420mV p.p. square.

The 13 and 18V voltages are fine modulated by the 22kHz, when this option is selected (~ 100mV p.p.)

The naming is incorrect on the v2.0 board as LNB1 is Tuner B and LNB2 is Tuner A (see Figure 10 Card Connections V2 BATC).

### Bill of material

See next page  
remote\_supply.docx

## Remote power supply for MiniTiouners

### Bill of material

; Date=19.janvier.2019 13:55

; Auteur= F5XG

;

Pos	Qty	Name	Value	Case	Provider
1	2	C1,C2	<a href="#">SMD TAN.10/16</a>	Tantalum capacitor SMD 10 $\mu$ F 16 VDC	Reichelt
2	1	C3	<a href="#">SMD TAN.22/20</a>	Tantalum capacitor SMD, 22 $\mu$ F/20 V	Reichelt
3	1	C4	<a href="#">KEM COG1206 100N</a>	1206_capacitor	Reichelt
4	1	C5	<a href="#">PS 25/8G BR</a>	Straight connector for PCB, 8 pins	Reichelt
5	3	D1,D2,D3	<a href="#">B 140 F</a>	Schottky Diodes SMD DO214AC/SMA	Reichelt
6	1	D4	<a href="#">P6SMB 20CA SMD</a>	Surge protection diode 20V, DO-214AA	Reichelt
7	1	IC1	<a href="#">RT5047</a>	SO8_SOT96-1_EP	ebay
8	1	L1	<a href="#">L-PISM 10<math>\mu</math></a>	Power inductance SMD, PISM	Reichelt